

Lab 8: Rotary Dial and PWM Signals



National Chiao Tung University
Chun-Jen Tsai
11/20/2015

Lab 8: Rotary Dial and PWM Signals


- ❑ In this lab, you will design a circuit to control the brightness of the LEDs through the rotary dial
- ❑ You will demo the design to your TA during the lab hours on 11/30

Control of LED Brightness

- ❑ The LED device in the Spartan-3e Starter Board can only be fully lit (full power) or turned off (zero power), you can not set it to different levels of brightness
- ❑ To trick your eyes to see different levels of brightness, you can send a Pulse Width Modulation (PWM) signal to its power input
 - The PWM signal will turn the LED on-an-off quickly such that the persistence of human visions will not see any flickering but different levels of brightness

A PWM Signal

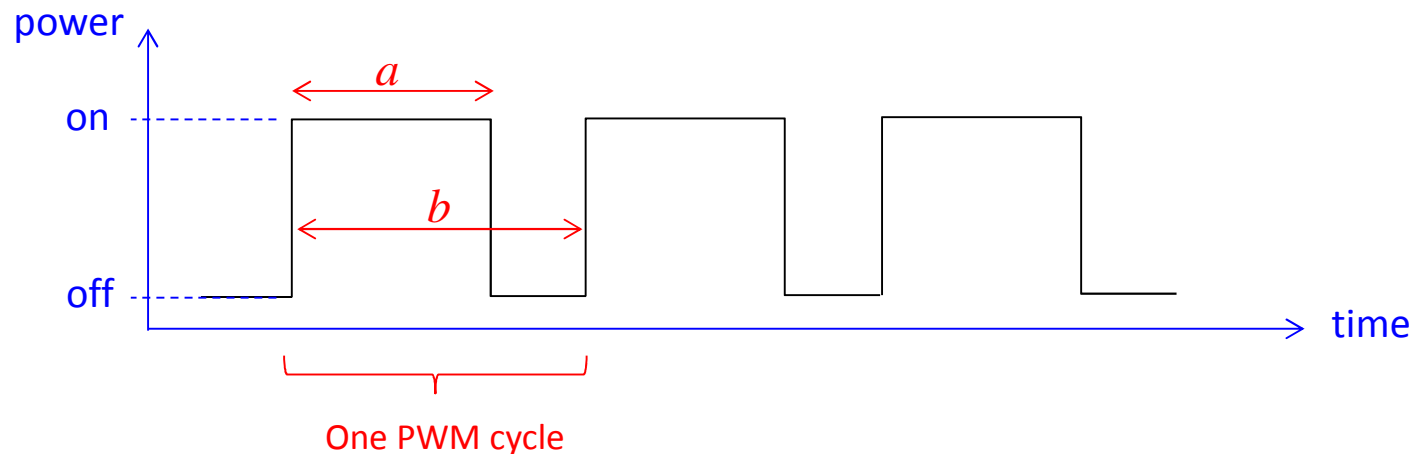
- ❑ A PWM signal is simply a square wave signal:



- ❑ Duty-cycle: the percentage of one cycle of PWM that is in “on” state (i.e., $(a/b) \times 100\%$ in the figure)
 - 50% duty-cycle means the signal is “on” half of the time


PWM Control of Brightness

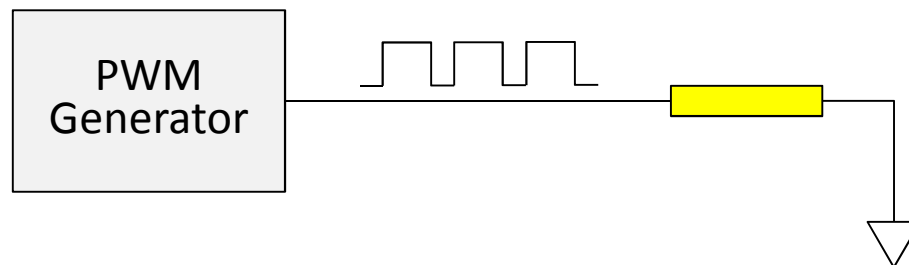- ❑ Persistence of visions make most people do not see flickering when the LCD is switching faster than 60 Hz
- ❑ We can use a 60 Hz (or higher) PWM signal to control the brightness of an LED
 - The PWM duty cycle determines the brightness of the LED
 - If you see flickering, raise the frequency to, say, 120Hz



Rotary Dial Control

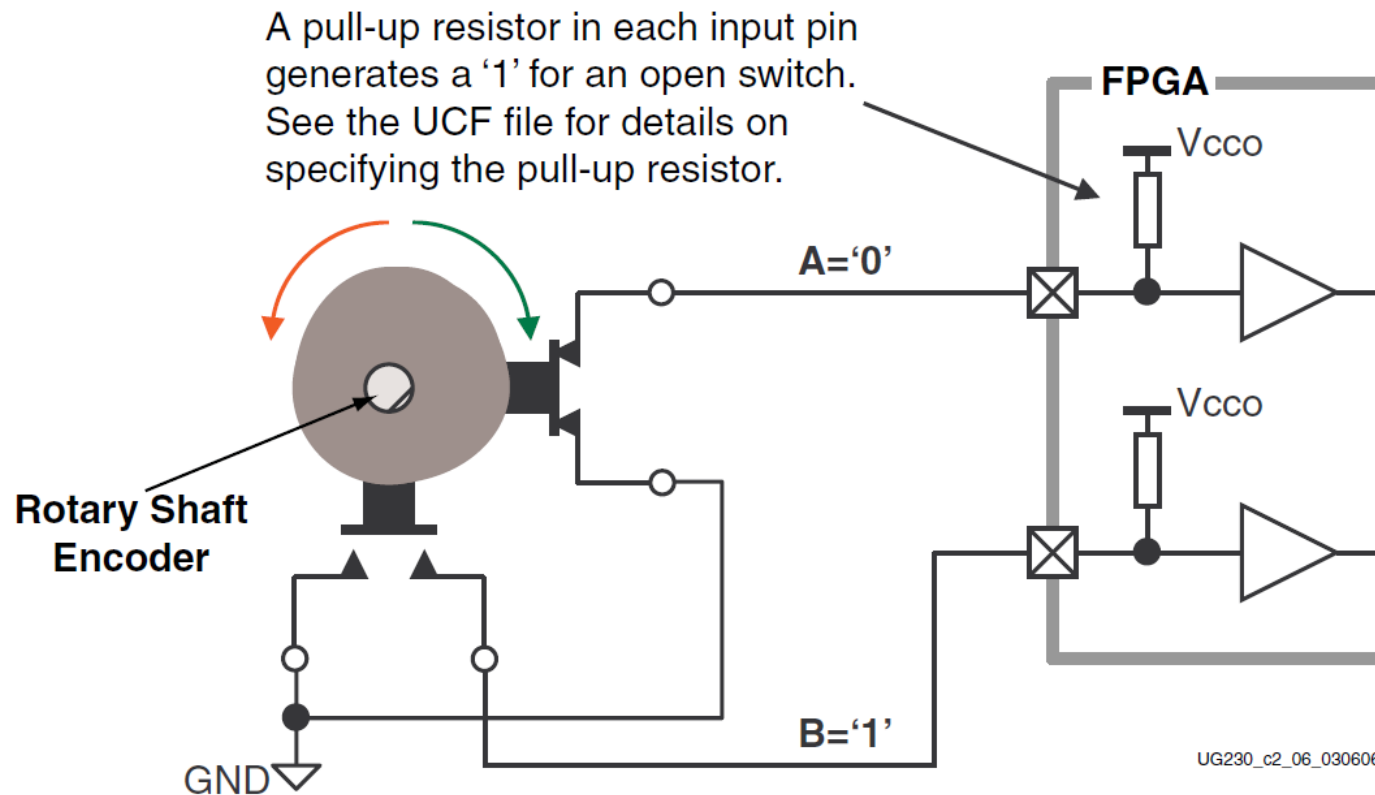- ❑ There is a rotary dial on the Spartan-3e board:



Rotary Controller


- ❑ A rotary controller module will be provided to you:

rotary_q1


Set ('1') when A is High and B is High
Reset ('0') when A is Low and B is Low.

rotary_q2

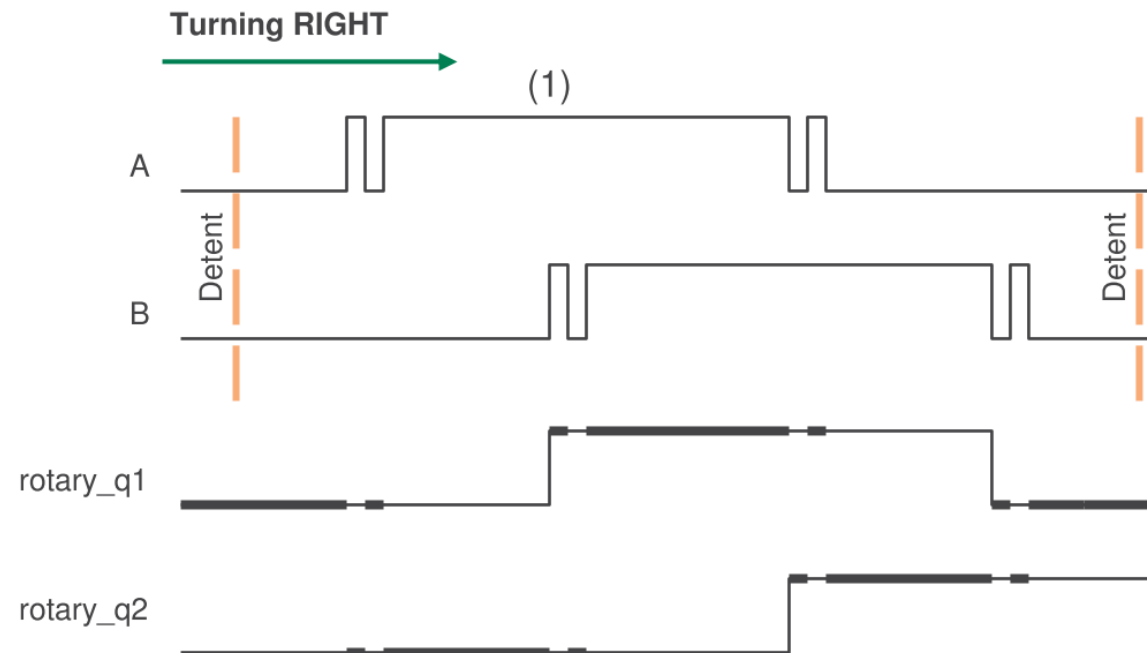Set ('1') when A is Low and B is High
Reset ('0') when A is High and B is Low.



Rotary Controller Waveform Examples

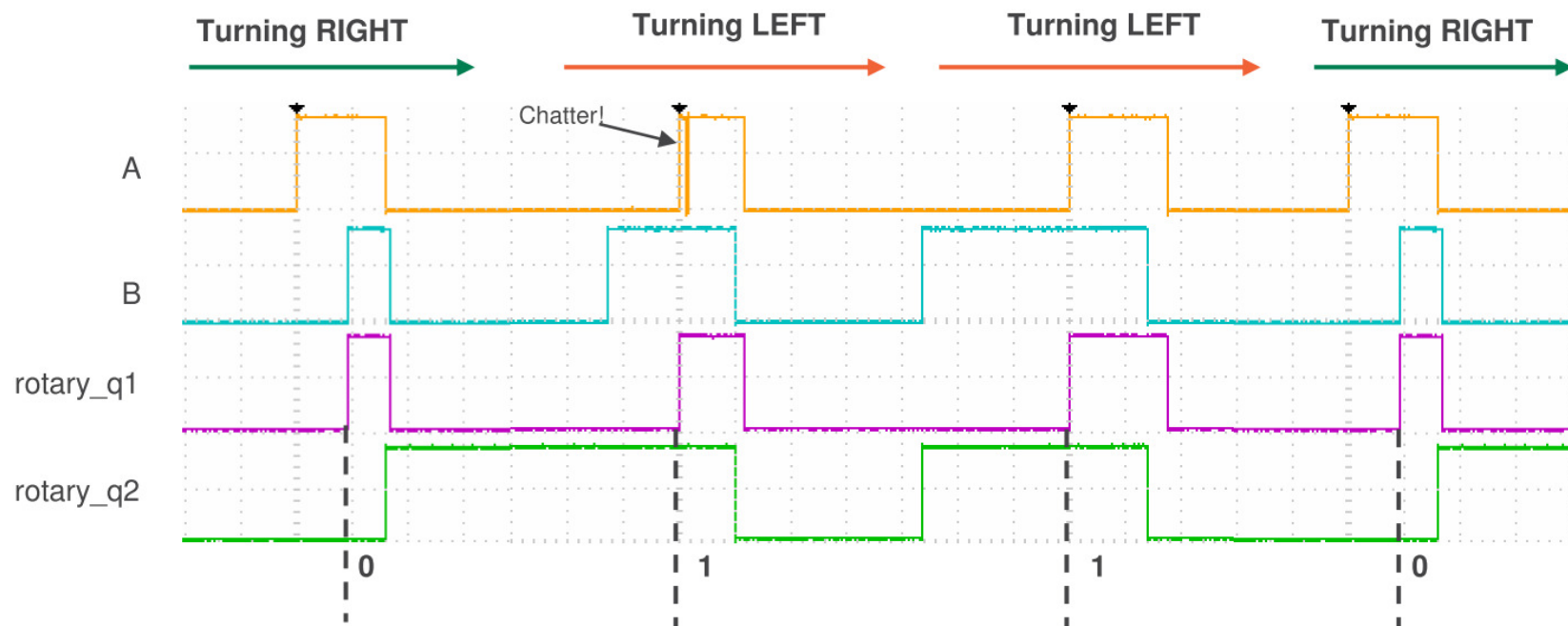

Rotary Controller Specification

- ❑ The controller module has five ports:

```
module Rotation_direction(  
    input CLK,  
    input ROT_A,  
    input ROT_B,  
    output reg rotary_event,  
    output reg rotary_right);
```

- CLK is the 50MHz system clock
- ROT_A and ROT_B are the two ports connect to the rotary pins
- rotary_event == 1 means the user is turning the rotary
- rotary_right == 1 means turning right, 0 means turning left

What You Need to Do for Lab 8

- ❑ Design a circuit to read the rotary input and use it to control the duty cycle of the PWM signal that feed to LED 4
 - At reset, the duty cycle set to 0%
 - Turn rotary right increase the duty cycle (hence the brightness)
 - Turn rotary left decrease the duty cycle
 - The duty cycle falls between 0% to 100%
- ❑ You must make your brightness control as smooth as possible

References

- ❑ Ken Chapman, *Rotary Encoder Interface for Spartan-3E Starter Kit*, Feb. 2006:
 - http://www.xilinx.com/products/boards/s3estarter/files/s3esk_rotary_encoder_interface.pdf